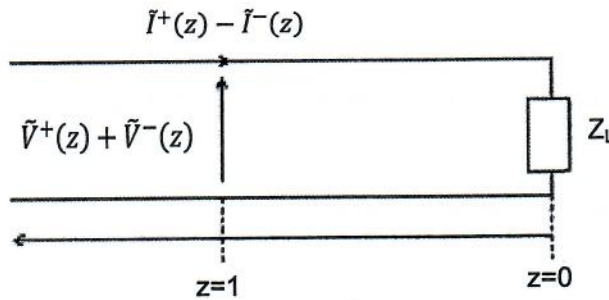


1. Consider the following **lossless** transmission line of characteristic impedance Z_0 . The origin of the line is taken at the position of the load.



Where $\tilde{I}^+(z)$, $\tilde{I}^-(z)$ are the position-dependent incident and reflected currents, and $\tilde{V}^+(z)$, $\tilde{V}^-(z)$ the incident and reflected voltages. Z_L is the load impedance.

- (a) Show that the voltage reflection coefficient at the load, Γ_L , is given by the relation

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

(5 marks)

- (b) The transmission line is operating at a frequency of 20 GHz with a characteristic impedance $Z_0 = 50 \, \Omega$. The load of the line is a resistance of $100 \, \Omega$ itself in series with a capacitance of 3 pF.

- (i) Calculate the reflection coefficient (magnitude and phase) and Voltage Standing Wave Ratio (VSWR) at the load.

(6 marks)

- (ii) Using a Smith chart, determine the position of first voltage maximum from the load.

(6 marks)

/Cont...

/Cont...1.

- (c) The following measurements of a transmission line of characteristic impedance $Z_0 = 50 \Omega$ are provided:

The first voltage maximum is occurring at 5 cm from the load.


The voltage standing wave ratio is $VSWR = 4$

The distance between adjacent voltage maxima is 20 cm.

- (i) Using a Smith chart, determine the value of the normalised load impedance, z_L , and deduce the load impedance, Z_L .
(4 marks)

- (ii) Using the Smith chart, determine the magnitude of the voltage reflection coefficient
(4 marks)

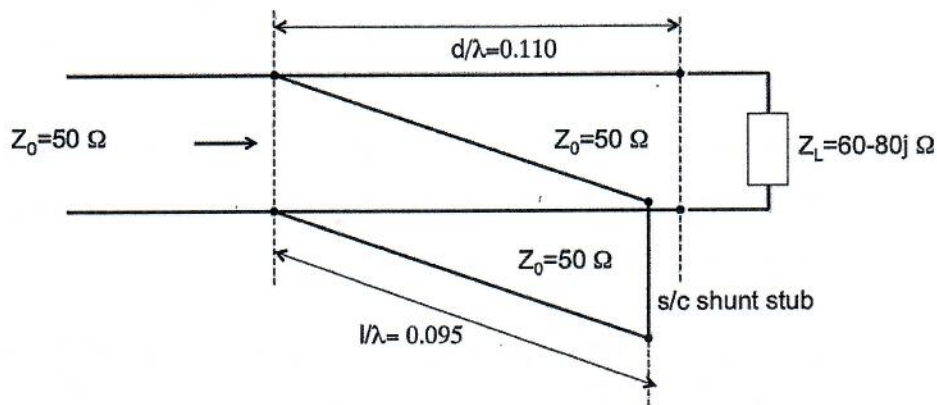2. Consider a load impedance $Z_L = 60 - j80 \Omega$ connected to a transmission line of characteristic impedance $Z_0 = 50 \Omega$. The circuit has been matched to the load using a single stub short-circuited (s/c) element of length 0.095λ and a transmission line of length 0.110λ according to the figure given below:



- (a) By using a Smith chart, verify that the single-stub, short-circuited, shunt matching network is effectively matching this load to a 50Ω impedance transmission line, in other words $Z_{in} = Z_0$.

Note: results are approximate.

(8 marks)

- (b) Using a Smith chart, show that there is another matching solution which uses a transmission line of length $d = 0.260\lambda$ and a single stub, short-circuited, shunt matching network of length $l = 0.405\lambda$.

(8 marks)

/Cont...

/Cont...2.

- (c) Assuming that the load is matched at 2 GHz and that the load consists of a resistor and capacitor in series.

- (i) Calculate the values of the resistance and capacitance.

(3 marks)

- (ii) The magnitudes of the input reflection coefficient, $|Γ_{in}|$, for these two matching networks as a function of frequencies ranging from 1 to 3 GHz can be given as below.

	First matching network	Second matching network
f = 1 GHz	0.95	0.78
f = 2 GHz	0	0
f = 3 GHz	0.8	0.45

- (A) Plot on the same graph, $|Γ_{in}|$ as a function of f for both matching networks.

(2 marks)

- (B) Which matching network would you choose? Justify your answer.


(3 marks)

3. (a) Label ALL of the following on a blank Smith Chart:

- (i) Infinite impedance,
- (ii) Infinite admittance,
- (iii) zero impedance,
- (iv) zero admittance,
- (v) $g = 1$ circle,
- (vi) location (or locations) defining no reflections, and
- (vii) location (or locations) for a standing wave ratio of 2.

(7 marks)

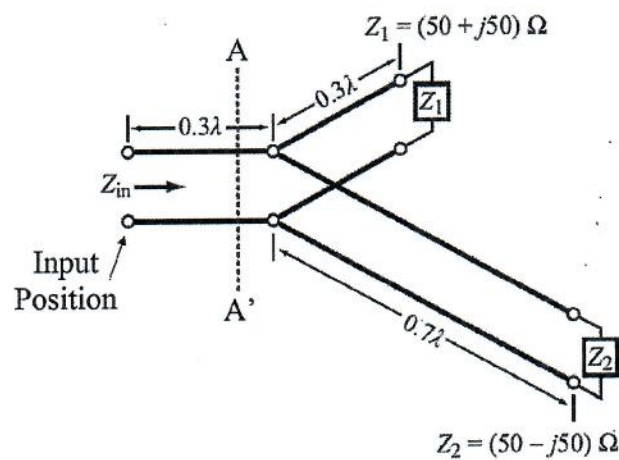(b) See the transmission line circuit show in the Figure below. All lines are lossless with $Z_0 = 50 \Omega$. Note: Part (a) is not needed for parts (b), (c), and (d).



Using the Smith Chart, determine Z_{in} .

(8 marks)

/Cont...

/cont...3.

- (c) Verify your above solution by using equations and calculations; i.e. NOT by using the Smith Chart.

(5 marks)

- (d) Now use the Smith Chart to develop an equivalent circuit by placing a complex load at the position AA' which is 0.75λ away from the input of the transmission line.

(5 marks)

4. (a) Draw the circuit diagram for an equal-split Branch line hybrid coupler. You can use basic transmission line sections as well. This coupler is to connect to other transmission lines which have a characteristic impedance of 75 Ohms.

(1 mark)

- (b) Make sure to include and clearly label the following on your circuit:

- (i) The important transmission line impedances,

(1 mark)

- (ii) The isolated and the through ports,


(1 mark)

- (iii) Any critical lengths.

(2 marks)

The following question parts are not related to parts (a) through (b).

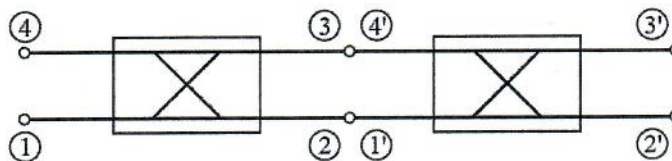- (c) Two identical 90 degree hybrid couplers, both with a coupling value $C = 8.34$ dB, are connected as shown below. You can consider the input voltage at port 1, on the left side, to be $V_1^+ = 1 \text{ V} \angle 0^\circ$.



- (i) Find the resulting output voltage amplitudes and phases at ports 2 and 3 (between the couplers), relative to the given input voltage V_1^+ .

(10 marks)

/Cont...

/Cont...4(c)

- (ii) Find the resulting output voltages at ports 2' and 3' (at the end of the second coupler), relative to the given input voltage V_1^+ .
(10 marks)

END OF PAPER